
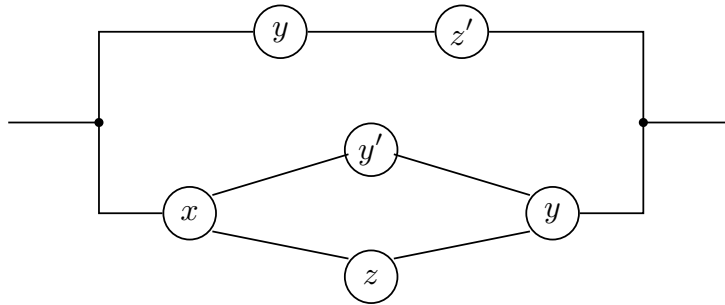


Tutorial 7 Week 8

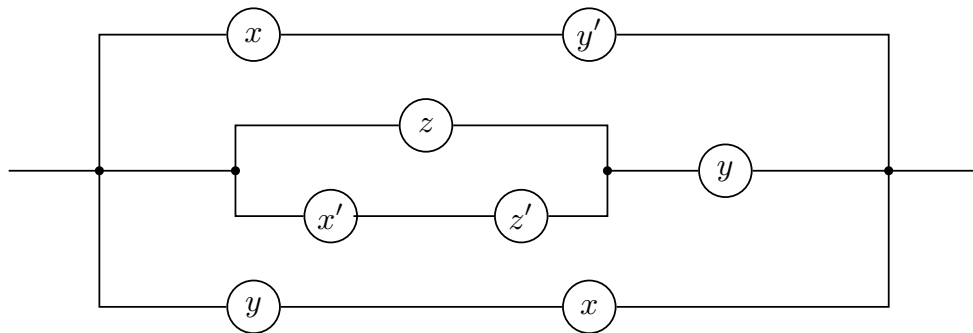1. Write a Boolean expression and the Boolean function for the switching circuit:



2. Write a Boolean expression and the Boolean function for the switching circuit:



3. Write down Boolean expressions in disjunctive normal form which represent the following Boolean functions and then find their corresponding switching circuits.

(i)	x	y	z	$f(x, y, z)$	(ii)	x	y	z	$f(x, y, z)$
	1	1	1	0		1	1	1	0
	1	1	0	1		1	1	0	1
	1	0	1	1		1	0	1	1
	1	0	0	1		1	0	0	0
	0	1	1	0		0	1	1	1
	0	1	0	1		0	1	0	0
	0	0	1	0		0	0	1	0
	0	0	0	1		0	0	0	0

4. Find a Boolean expression and a switching circuit for each of the following Boolean functions.

(i)

x	y	$f_1(x, y)$
1	1	0
1	0	0
0	1	0
0	0	0


(ii)

x	y	$f_2(x, y)$
1	1	1
1	0	1
0	1	1
0	0	1

5. Write down the other 14 Boolean functions of two variables and write down their Boolean expressions in disjunctive normal form.


Problem Set 7

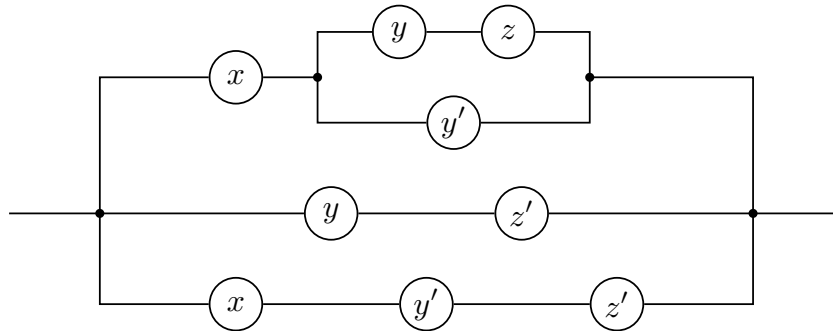1. Consider the following switching circuit.



- (i) Write down a Boolean expression which represents the switching circuit.
- (ii) Draw up the Boolean function corresponding to the switching circuit and write down the corresponding Boolean expression in disjunctive normal form.

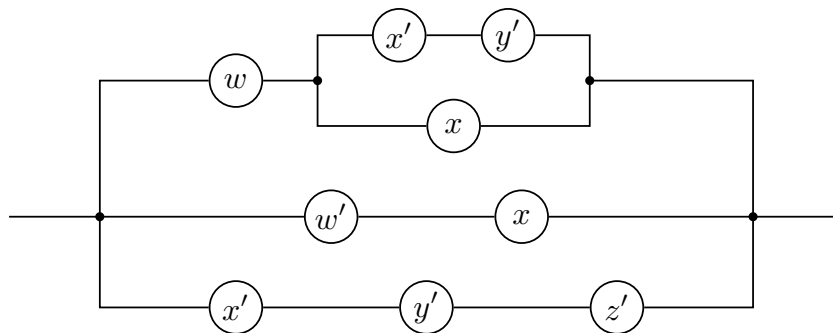2. Consider the following switching circuit.



- (i) Write down a Boolean expression which represents the switching circuit.
- (ii) Draw up the Boolean function corresponding to the switching circuit and write down the corresponding Boolean expression in disjunctive normal form.